

# Main Template

Ethan Anthony

## CONTENTS

<b>1</b>	<b>Introduction</b>	<b>2</b>
1.1	Categorization of Components . . . . .	2
1.2	Overview of Concepts . . . . .	2
1.2.1	Charge and Current . . . . .	2
1.2.2	DC vs. AC . . . . .	3
1.2.3	Power and Energy . . . . .	3
1.3	Circuit Elements . . . . .	4
1.4	Basic Laws . . . . .	4
1.4.1	Ohm's Law . . . . .	4
1.4.2	Nodes, Branches, Loops . . . . .	4
1.4.3	Kirchhoff's Laws . . . . .	5

# 1 INTRODUCTION

## 1.1 CATEGORIZATION OF COMPONENTS

Rather than trying to understand full circuits at once, it is easier to break them into two groups: **passive** components and **active** components.

### Passive Components

1.1

Passive components are ones that don't require any power supply to operate. For example, a resistor or a capacitor are both passive components.

### Active Circuits

1.2

Active components require power to operate. In other words, they need to be connected to a power supply to function. Logic gates (74LSXX) are active since they require a power supply.

Another way to divide components is between **linear** and **non-linear**.

### Linear Components

1.3

Linear components are... They also can be subdivided into components that store energy (capacitors and inductors) and components that dissipate energy (resistors).

### Non-Linear Components

1.4

...

## 1.2 OVERVIEW OF CONCEPTS

### 1.2.1 CHARGE AND CURRENT

#### Charge

1.5

Charge ( $Q$ ) is an electrical property of the atomic particles of which matter consists, measured in coulombs ( $C$ ).

$$Q(t) = \int i(t) dt$$

When charged particles move in space over time, such as throughout a wire in a circuit, an electrical current is generated.

#### Electric Current

1.6

Electric current ( $I$ ) is the time rate of change of charge, measured in amperes ( $A$ ).

$$i(t) = \frac{dQ}{dt}$$

Current is simply a rate of change of a charge, and thus the two are related as the others' derivative/integral.

### 1.2.2 DC vs. AC

#### Direct Current

1.7

A direct current (dc) flows only in one direction and can be constant or time varying.

There are two ways of describing the *direction* in which the electrons flow in a direct current: **conventional flow** and **electron flow**. Both are shown in Figure 1.

#### Alternating Current

1.8

An alternating current (ac) is a current that changes direction with respect to time.

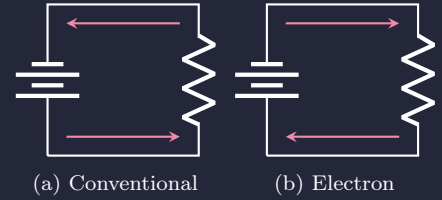


Figure 1: Electron Flow in Direct Currents

#### Voltage

1.9

Voltage (or *potential difference*) is the energy required to move a unit charge from a reference point (-) to another point (+), measured in Volts (V).

$$v(t) = v_b - v_b = \frac{dw}{dQ} = \frac{dE}{dQ}$$

### 1.2.3 POWER AND ENERGY

#### Power

1.10

Power is the time rate of expending or absorbing energy measured in watts (W). It is the rate of change of energy.

$$p(t) = \frac{dE}{dt} = \frac{dE \cdot dQ}{dt \cdot dQ} = \frac{dE}{dQ} \cdot \frac{dQ}{dt}$$

$$p = v \cdot i$$

#### Energy

1.11

Energy is the capacity to do work measured in Joules (J).

$$E(t) = \int p(t) dt$$

Again, these two values are related as the derivative/integral of the other.

## 1.3 CIRCUIT ELEMENTS

### Ideal Independent Source

1.12

An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit elements.

### Ideal Dependent Source

1.13

Also called an *Ideal Controlled Source*, this is an active element in which the source quantity is controlled by another voltage or current.

There are four types of dependent sources:

1. Voltage Controlled Voltage Source (VCVS)
2. Voltage Controlled Current Source (VCCS)
3. Current Controlled Voltage Source (CCVS)
4. Current Controlled Current Source (CCCS)

## 1.4 BASIC LAWS

### 1.4.1 OHM'S LAW

**Ohm's Law** states that the voltage  $V$  across a resistor is *directly* proportional to the current  $I$  flowing through the resistor.

#### Ohm's Law

$$R = \rho \cdot \frac{l}{A}$$

1.1

When there is current flowing through a wire with resistance approaching zero, a **short circuit** is created. Conversely, an **open circuit** is where the resistance in a circuit approaches infinity.

Resistance and conductance are inversely related. It is the ability of an element of conduct electric current; it is measured in mhos or siemens ( $S$ ).

### 1.4.2 NODES, BRANCHES, LOOPS

#### Branch

1.14

Represents a single element in a circuit such as a resistor or power supply.

#### Node

1.15

The point of connection between two or more branches.

**Loop****1.16**

A loop is any *closed* path in a circuit. Generally, loops are defined as the smallest possible path.

By analyzing the nodes connection branches of a circuit, elements can be found to be in parallel or in series.

**Parallel****1.17**

Elements are in parallel if they share two nodes.

**Series****1.18**

Elements are in series if they *exclusively* share a node.

It is possible for elements to be neither in series or in parallel. These situations aren't problematic, but require somewhat different techniques to analyze.

**1.4.3 KIRCHHOFF'S LAWS****Kirchhoff's Current Law****1.19**

Kirchhoff's Current Law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero:

$$\sum_{n=1}^{N_{branch}} i_n = 0$$

**Kirchhoff's Voltage Law****1.20**

Kirchhoff's Voltage Law (KVL) states that the algebraic sum of all voltages around a closed path is zero:

$$\sum_{m=1}^{M_{branch}} v_m = 0$$